

MMIC Chip Design

Microwave Design and Measurements (EERF 6396)

Prof. Dr. Randall E. Lehmann

The University of Texas at Dallas

Submitted By

Niyati Sanandiya

(2021317640)

1. Introduction

A. What did you do?

- Design A: Ideal Butterworth high-pass lumped element filter at cut off frequency 10 GHz.
- Design B: MMIC Butterworth high-pass on GaAs at cut off frequency 10 GHz.

2. Design and Simulations

Design A: Ideal Butterworth high-pass lumped element filter


Parameter	Design Goal
f_c (GHz)	10.0
Rejection at 5GHz (dB)	≥ 30
No. of elements (N, odd)	Minimum
Pi topology	
Z_G and $Z_L = 50\Omega$	

- Number of elements required was found to be 5 from the graph (normalized frequency vs. attenuation) to get minimum 30 dB attenuation at 5 GHz, where cut off frequency is 10 GHz.
- The value of inductances and capacitances were calculated from the below equations:


$$L = \frac{R}{2 * \pi * G_n * F_c}$$

$$C = \frac{1}{2 * \pi * F_c * G_n * R}$$

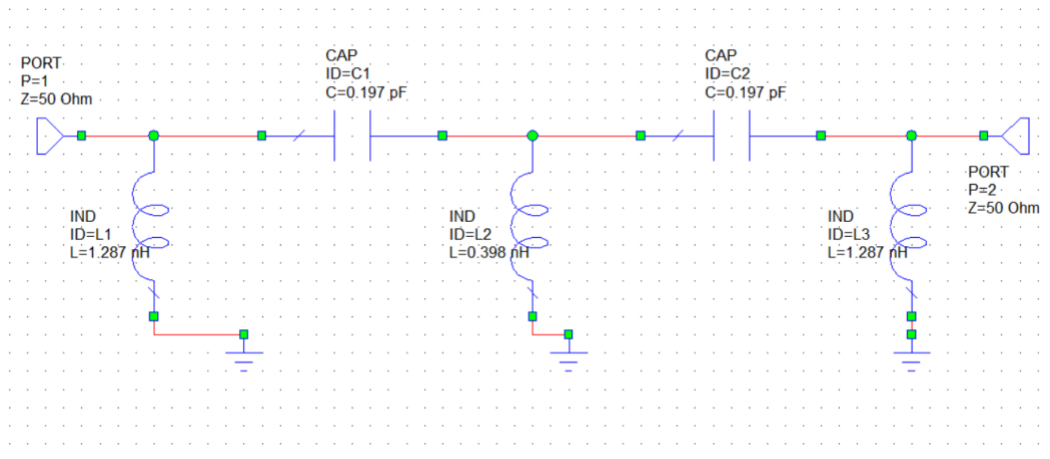1. Circuit schematic with component values:



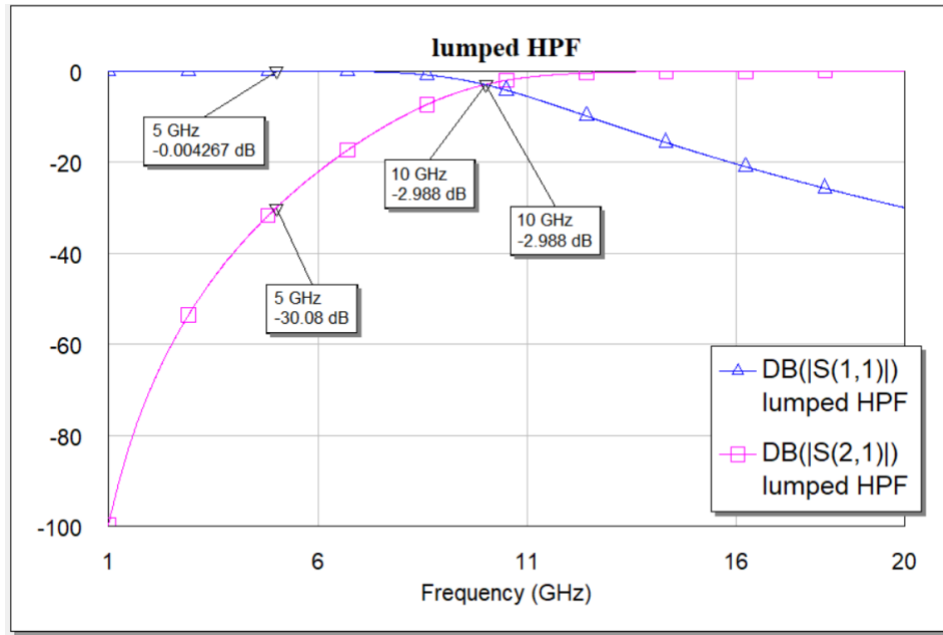2. MWO simulation for S11 and S21 (in dB) over a frequency range 1-20GHz



3. Compliance Matrix

Parameter	Design Goal	MWO Simulation Performance	Compliant (Yes/No)
Cut-off frequency (f_c)(GHz)	10 GHz	10 GHz	Yes
Rejection @ 5 GHz (dB) Ideal	≥ 30 dB	30.08	Yes
No. of elements (N, odd)	Minimum	5	Yes

Design B: MMIC Butterworth high-pass filter on GaAs


Parameter	Design Goal
f_c (GHz)	10.0
Rejection at 5GHz (dB) (actual $ S_{21} $)	≥ 25
No. of elements (N, odd)	Minimum
Tee topology	
Z_G and $Z_L = 50\Omega$	
MMIC Chip Size (sq mm)	Minimum

- Number of elements required was found to be 5 from the graph (normalized frequency vs. attenuation) to get minimum 25 dB rejection at 5 GHz, where cut off frequency is 10 GHz.
- The value of inductances and capacitances were calculated from the below equations:


$$L = \frac{R}{2 * \pi * G_n * F_c} \quad C = \frac{1}{2 * \pi * F_c * G_n * R}$$

- Ground pads were placed on both sides of the RF signal pad to enable G-S-G autoprobing capability.

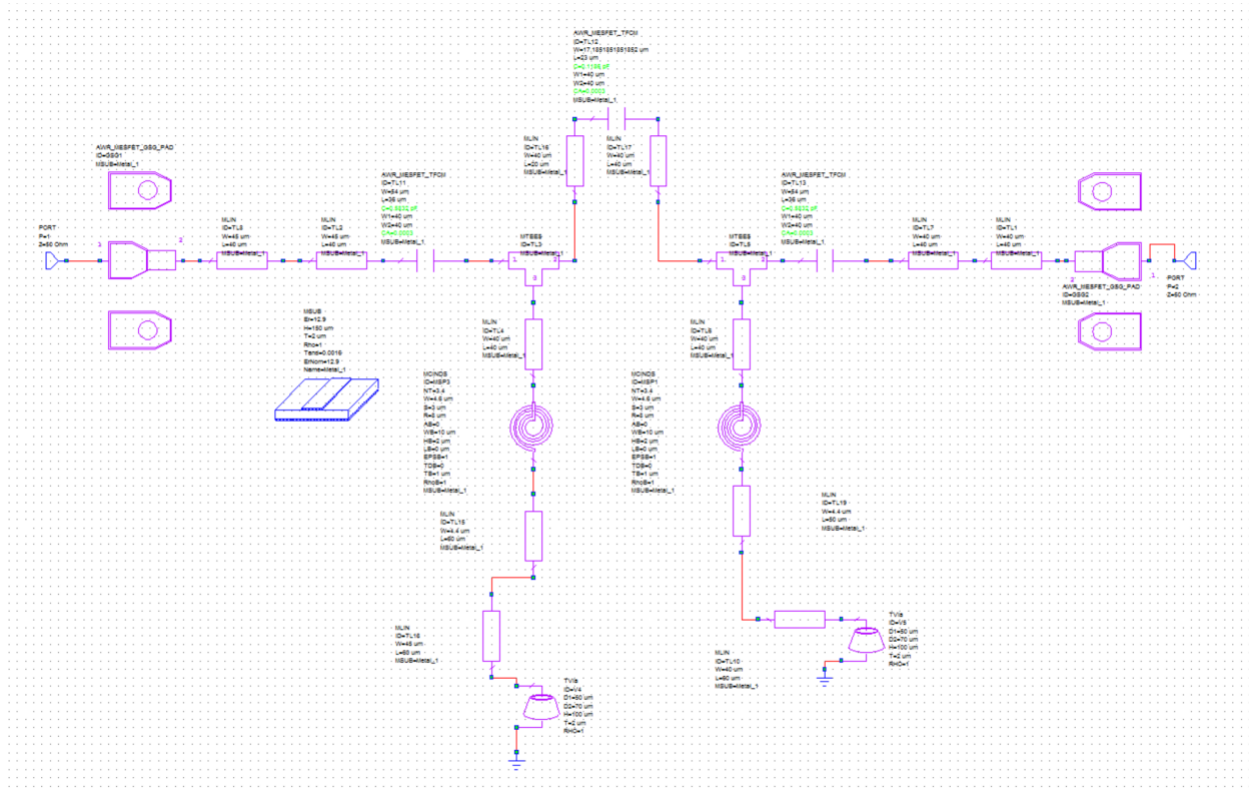1. Circuit schematic with component values




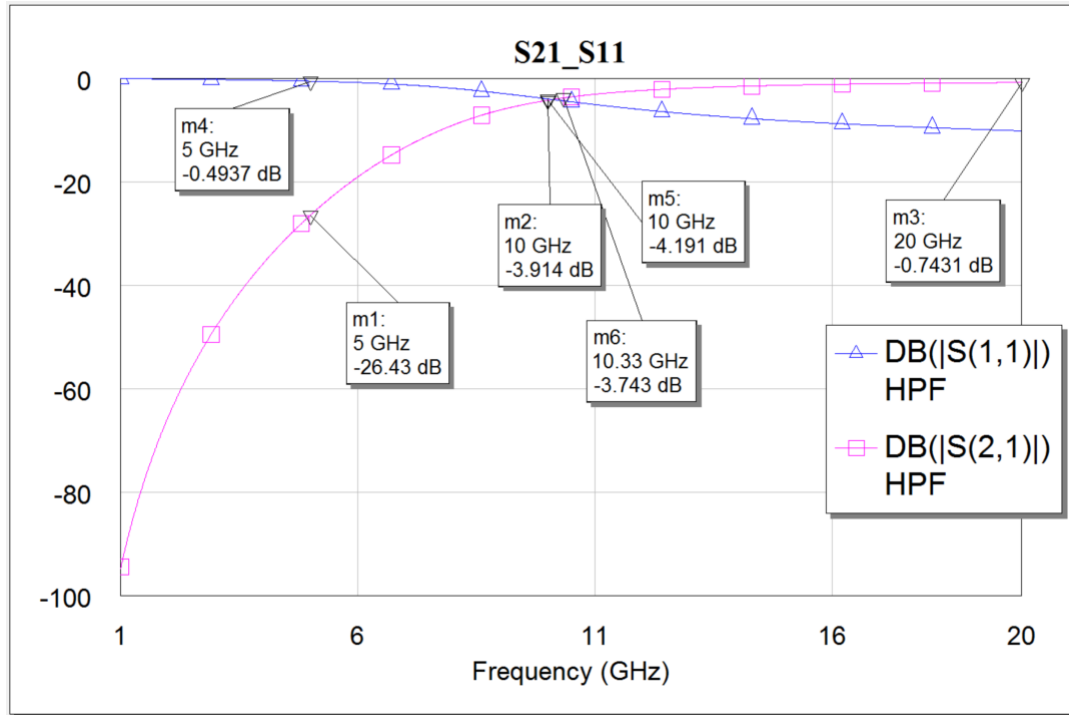2. MWO simulation for S11 and S21 (in dB) over a frequency range 1-20GHz



The cutoff frequency is at 10.33 GHz where S21 is -3 dB down from its maximum.

3. MMIC chip layout

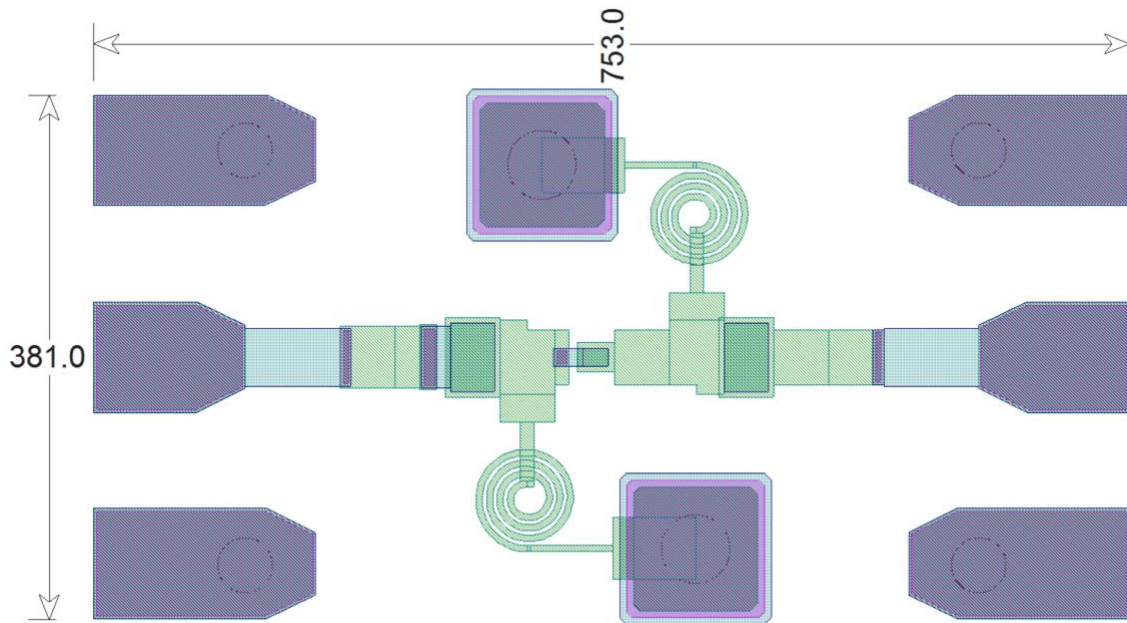

4. Compliance matrix

Parameter	Design Goal	MWO Simulation Performance	Compliant (Yes/No) (+/- 5%)
Cut-off frequency (f _c)(GHz)	10 GHz	10.33 GHz	Yes
Rejection @ 5 GHz GHz (dB)	>= 25 dB	26.43	Yes
No. of elements (N, odd)	Minimum	5	Yes

5. Summary

Q1. Calculation of how many filters you would expect to yield on a 150mm diameter wafer.

$$\text{Chip Area} = 381 * 753 \mu\text{m}^2 = 0.286893 \text{ mm}^2$$

- a. Assume the outside 10mm of the wafer cannot be used

If outside 10mm of the wafer cannot be used, then the radius will be 65 mm.

$$\text{Area with 65mm} = 13273.22 \text{ mm}^2.$$

- b. Assume you lose another 5% of the (total) wafer area for process control monitor chips

$$\text{Area} = 0.95 * 13273.22 = 12609.559 \text{ mm}^2.$$

- c. Assume you have a 90% total process & RF yield to calculate your final number of available chips from one completed wafer.

$$\text{Wafer Area} = 0.90 * 12609.559 \text{ mm}^2 = 11348.6 \text{ mm}^2.$$

$$\text{Number of filters} = 11348.6 \text{ mm}^2 / 0.286893 \text{ mm}^2. = 39556.91$$

- MMIC HPF was designed which has cut-off frequency around 10 GHz with rejection of 26.43 dB at 5 GHz.
- 39556 filters are expected to be yield on a 150mm diameter wafer.